

## APPLICATION NOTE

# APN1006: A Colpitts VCO for Wideband (0.95–2.15 GHz) Set-Top TV Tuner Applications

## Introduction

Modern set-top DBS TV tuners require high-performance, broadband voltage control oscillator (VCO) designs at a competitive cost. To meet these goals, design engineers are challenged to create high-performance, low-cost VCOs.

The Colpitts oscillator is a traditional design used for many VCO applications. Designing a broadband Colpitts oscillator with coverage from 1–2 GHz requires the selection and interaction of an appropriate varactor diode for its resonator. This application note describes the design of a broadband Colpitts VCO that incorpo-

rates the SMV1265-011 varactor diode. This varactor diode was specifically developed at Skyworks for this application. The VCO design, based on Libra Series IV simulation, shows good correlation between measured and simulated performance. This application note includes a board layout and materials list.

## VCO Model

Figure 1 shows the VCO model built for open loop analysis in Libra Series IV.

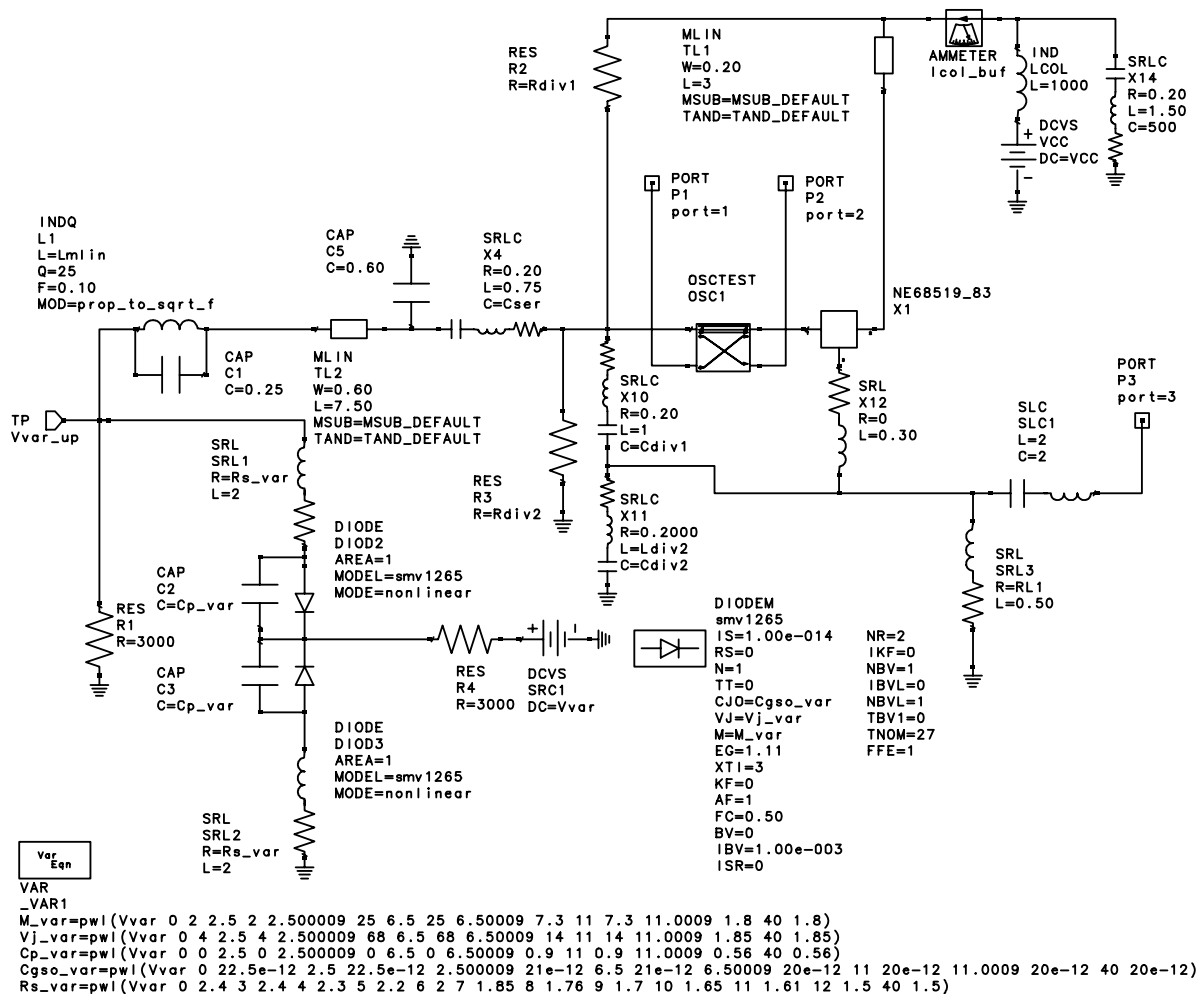


Figure 1. VCO Model Built for Open Loop Analysis in Libra Series IV

This circuit schematic, which is a simple Colpitts structure, uses a series back-to-back connection of two SMV1265-011 varactors instead of a single varactor. This connection allows lower capacitance at high voltages, while maintaining the tuning ratio of a single varactor. The back-to-back varactor connection also helps reduce distortion and the effect of fringing and mounting capacitances. These parasitic capacitances are included in the model as  $C_5$ , valued at 0.6 pF. This value may change depending on the layout of the board.

DC bias is provided through resistors  $R_1$  and  $R_4$ , both 3 k $\Omega$ , which may affect phase noise, but allows the exclusion of chokes. This reduces costs and the possibility of parasitic resonances — the common cause of spurious responses and frequency instability.

The resonator inductance was modeled as a lossy inductor (with  $Q = 25$  at 100 MHz) in parallel with a capacitance of 0.25 pF. This is typical for a multilayer inductor of style 0603 (60 x 30 mil) footprint (TOKO Coils and Filters catalog). The inductor value of 5.6 nH was optimized to fit the desired 1–2 GHz frequency band. The DC blocking series capacitance ( $C_{SER}$ ) was modeled as an SRC network, including associated parasitics; it was selected at 1000 pF to avoid affecting the resonator ( $Q$ ).

The Colpitts feedback capacitances ( $C_{DIV1} = 1$  pF and  $C_{DIV2} = 1.62$  pF) were optimized to provide a flat power response over the tuning range. These values may also be re-optimized for phase noise if required.

The NEC NE68533 transistor was selected to fit the required bandwidth performance. Note: The circuit is very sensitive to the transistor choice (tuning range and stability) due to the wide bandwidth requirement. The output is supplied from the emitter load resistance ( $R_{L1}$ ) through the 2 pF coupling capacitor, modeled as a series SLC<sub>1</sub> component.

The microstrip line ( $TL_1$ ) simulates the design layout which may be incorporated in the resonator.

Figure 2 shows the Libra test bench. In the test bench, we define an open loop gain ( $K_u = V_{OUT}/V_{IN}$ ) as a ratio of voltage phasors at input and output ports of an OSCTEST component. Defining the oscillation point requires the balancing of input (loop) power to provide zero gain for a zero loop phase shift. Once the oscillation point is defined, the frequency and output power can be measured. Use of the OSCTEST2 component for the close loop analysis is not recommended, since it may not converge in some cases, and doesn't allow clear insight into understanding the VCO behavior. These properties are considered an advantage of modeling over a purely experimental study.

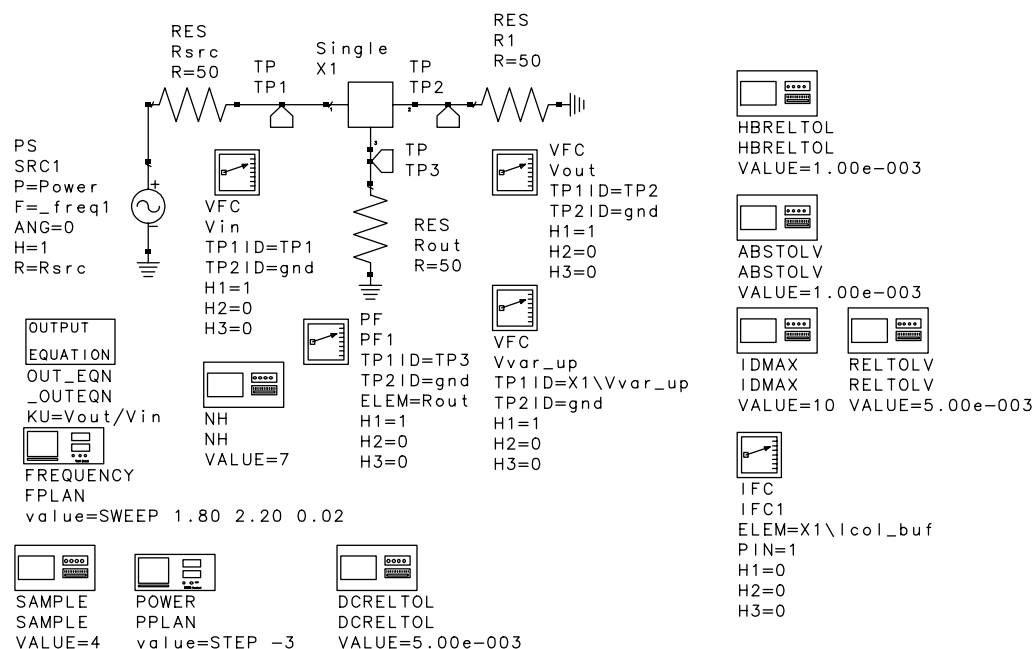


Figure 2. Libra Test Bench

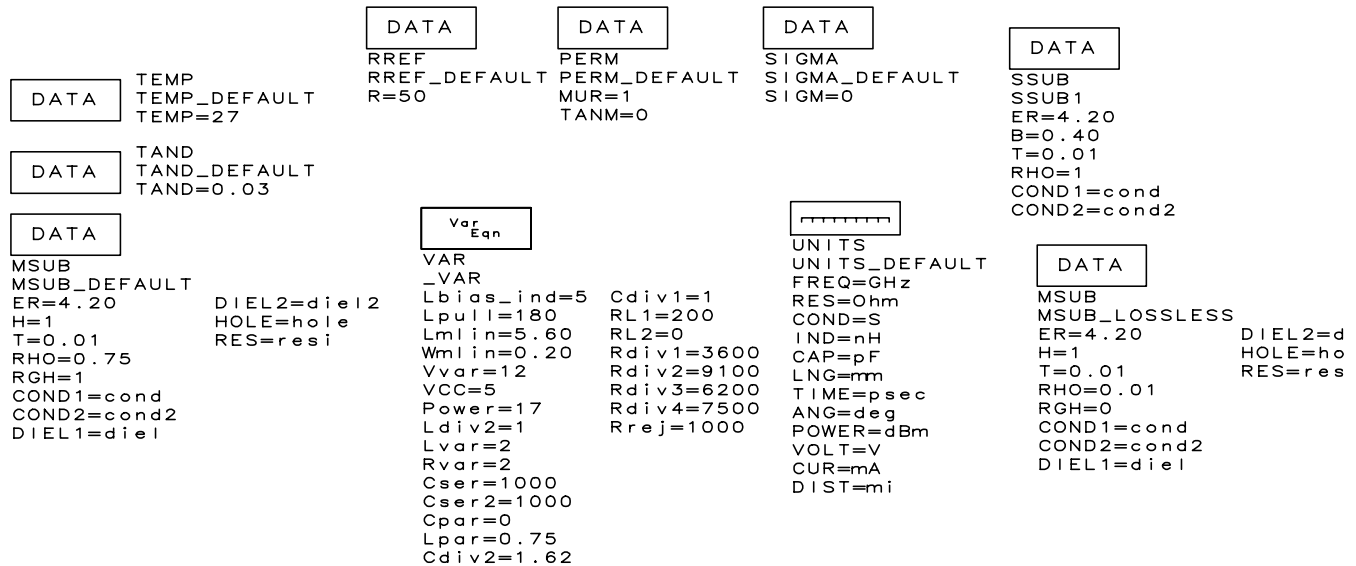


Figure 3. Default Test Bench

Figure 3 shows the default bench. The variables used for more convenient tuning during performance analysis and optimization are listed in a “variables and equations” component.

### SMV1265-011 SPICE Model

Figure 4 shows a SPICE model for the SMV1265-011 varactor diode, defined for the Libra IV environment, with a description of the parameters employed.

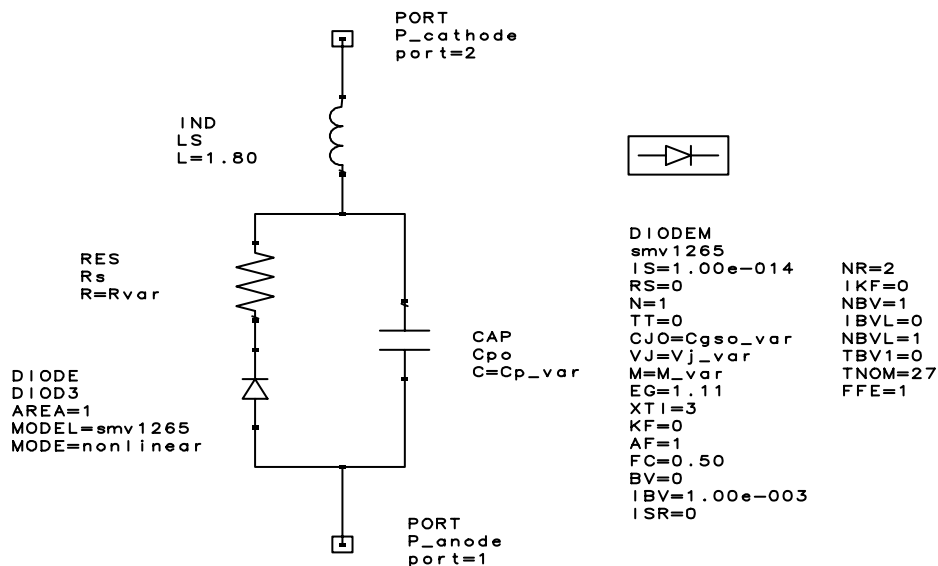


Figure 4. SMV1265-011 Libra IV SPICE Model

Parameter	Description	Unit	Default
IS	Saturation current (with N, determine the DC characteristics of the diode)	A	1e-14
R <sub>S</sub>	Series resistance	Ω	0
N	Emission coefficient (with IS, determines the DC characteristics of the diode)	-	1
TT	Transit time	S	0
C <sub>J0</sub>	Zero-bias junction capacitance (with V <sub>J</sub> and M, defines nonlinear junction capacitance of the diode)	F	0
V <sub>J</sub>	Junction potential (with V <sub>J</sub> and M, defines nonlinear junction capacitance of the diode)	V	1
M	Grading coefficient (with V <sub>J</sub> and M, defines nonlinear junction capacitance of the diode)	-	0.5
E <sub>G</sub>	Energy gap (with XTI, helps define the dependence of IS on temperature)	EV	1.11
XTI	Saturation current temperature exponent (with E <sub>G</sub> , helps define the dependence of IS on temperature)	-	3
KF	Flicker noise coefficient	-	0
AF	Flicker noise exponent	-	1
FC	Forward-bias depletion capacitance coefficient	-	0.5
B <sub>V</sub>	Reverse breakdown voltage	V	Infinity
I <sub>BV</sub>	Current at reverse breakdown voltage	A	1e-3
ISR	Recombination current parameter	A	0
NR	Emission coefficient for ISR	-	2
IKF	High injection knee current	A	Infinity
NBV	Reverse breakdown ideality factor	-	1
IBVL	Low-level reverse breakdown knee current	A	0
NBVL	Low-level reverse breakdown ideality factor	-	1
T <sub>NOM</sub>	Nominal ambient temperature at which these model parameters were derived	°C	27
FFE	Flicker noise frequency exponent		1

Table 1. Silicon Varactor Diode Default Values

Table 1 describes the model parameters. It shows default values appropriate for silicon varactor diodes which may be used by the Libra IV simulator.

According to the SPICE model in Figure 4, the varactor capacitance (C<sub>V</sub>) is a function of the applied reverse DC voltage (V<sub>R</sub>) and may be expressed as follows:

$$C_V = \frac{C_{J0}}{\left(1 + \frac{V_R}{V_J}\right)^M} + C_P$$

This equation is a mathematical expression of the capacitance characteristic. The model is accurate for abrupt junction varactors (SMV1400 series); however, the model is less accurate for hyperabrupt junction varactors because the coefficients are dependent on the applied voltage. To make the equation fit the hyperabrupt performances for the SMV1265-011, a piece-wise approach was employed. Here the coefficients (V<sub>J</sub>, M, C<sub>J0</sub>, and C<sub>P</sub>) are made piece-wise functions of the varactor DC voltage applied. Thus, the

whole range of the usable varactor voltages is segmented into a number of subranges each with a unique set of the V<sub>J</sub>, M, C<sub>J0</sub>, and C<sub>P</sub> parameters as given in the Table 2.

Voltage Range (V)	C <sub>J0</sub> (pF)	M	V <sub>J</sub> (V)	C <sub>P</sub> (pF)
0–2.5	22.5	2	4	0
2.5–6.5	21	25	68	0
6.5–11	20	7.3	14	0.9
11–up	20	1.8	1.85	0.56

Table 2. Varactor Voltages

These subranges are made to overlap each other. Thus, if a reasonable RF swing (one that is appropriate in a practical VCO case) exceeds limits of the subrange, the C<sub>V</sub> function described by the current subrange will still fit in the original curve.

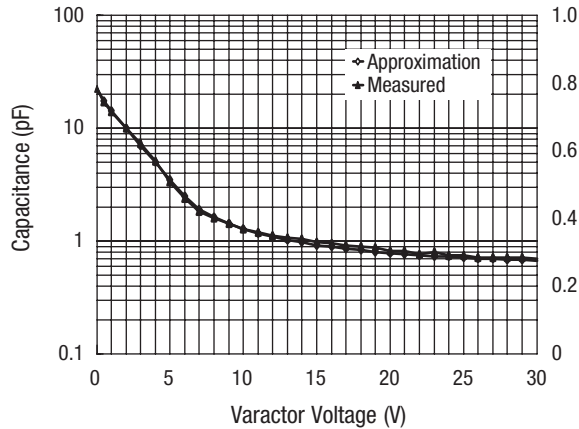


Figure 5. SMV1265 Capacitance vs. Voltage

Figure 5 demonstrates the quality of the piece-wise fitting approach.

Special consideration was given to the fit at the lowest capacitance range (high-voltage area) since it dramatically affects the upper frequency limit of the VCO.

To incorporate this function into Libra, the `pwl()` built-in function was used in the “variables” component of the schematic bench.

$M = \text{pwl}(V_{\text{VAR}} \ 0 \ 2 \ 2.5 \ 2 \ 2.500009 \ 25 \ 6.5 \ 25 \ 6.50009 \ 7.3 \ 11 \ 7.3 \ 11.0009 \ 1.8 \ 40 \ 1.8)$

$V_J = \text{pwl}(V_{\text{VAR}} \ 0 \ 4 \ 2.5 \ 4 \ 2.500009 \ 68 \ 6.5 \ 68 \ 6.50009 \ 14 \ 11 \ 14 \ 11.0009 \ 1.85 \ 40 \ 1.85)$

$C_P = \text{pwl}(V_{\text{VAR}} \ 0 \ 0 \ 2.5 \ 0 \ 2.500009 \ 0 \ 6.5 \ 0 \ 6.50009 \ 0.9 \ 11 \ 0.9 \ 11.0009 \ 0.56 \ 40 \ 0.56)$

$C_{J0} = \text{pwl}(V_{\text{VAR}} \ 0 \ 22.5 \ 2.5 \ 22.5 \ 2.500009 \ 21 \ 6.5 \ 21 \ 6.50009 \ 20 \ 11 \ 20 \ 11.0009 \ 20 \ 40 \ 20) \cdot 10^{12}$

Note: While  $C_P$  is given in picofarads,  $C_{J0}$  is given in farads to comply with the default nominations in Libra. (For more details regarding `pwl()` function see Circuit Network Items, Variables and Equations, Series IV Manuals, p. 19–15).

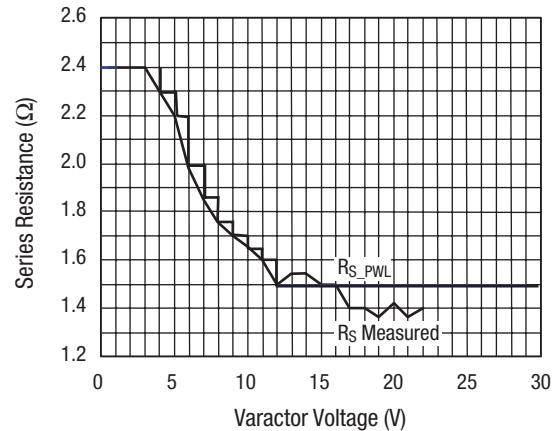


Figure 6. SMV1265 Resistance vs. Voltage

Since the epitaxial layer for this kind of hyperabrupt varactor has relatively high resistivity, the series resistance is strongly dependent on the reverse voltage applied to varactor junction. The value of series resistance ( $R_S$ ) measured at 500 MHz is shown in Figure 6, with a piece-wise approximation of  $R_S$  also given.

The piece-wise function may be used as follows:

$R_S = \text{pwl}(V_{\text{VAR}} \ 0 \ 2.4 \ 3 \ 2.4 \ 4 \ 2.3 \ 5 \ 2.2 \ 6 \ 2 \ 7 \ 1.85 \ 8 \ 1.76 \ 9 \ 1.7 \ 10 \ 1.65 \ 11 \ 1.61 \ 12 \ 1.5 \ 40 \ 1.5)$

Note: The `pwl()` function in Libra IV is defined for the evaluation of harmonic balance parameters rather than variables. Therefore, although series resistance was defined as dependent on reverse voltage, for harmonic balance it remains parametric and linear. The same applies to capacitance, which remains the same as in the original diode model, but its coefficients ( $V_J$ ,  $M$ ,  $C_{J0}$ , and  $C_P$ ) become parametric functions of the reverse voltage.

VCO Design Materials, Layout, and Performance

Figure 7 shows the VCO circuit diagram.

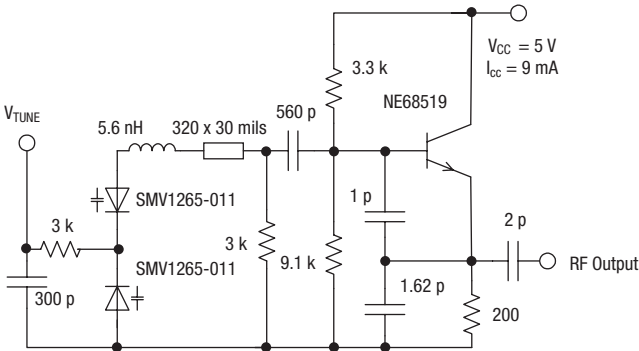


Figure 7. VCO Circuit Diagram

Table 3 shows the bill of materials used.

Designator	Part Type	Footprint
C <sub>1</sub>	0603AU561JAT9 (AVX)	0603
C <sub>2</sub>	0603AU2R0JAT9 (AVX)	0603
C <sub>3</sub>	0603AU561JAT9 (AVX)	0603
C <sub>4</sub>	0603AU201JAT9 (AVX)	0603
C <sub>5</sub>	0603AU1R0JAT9 (AVX)	0603
C <sub>6</sub>	0603AU1R6JAT9 (AVX)	0603
D <sub>1</sub>	NE68519 (NEC)	SOT-419
L <sub>1</sub>	LL1608-F5N6S (TOKO)	0603
R <sub>1</sub>	CR10-332J-T (AVX)	0603
R <sub>2</sub>	CR10-912J-T (AVX)	0603
R <sub>3</sub>	CR10-201J-T (AVX)	0603
R <sub>4</sub>	CR10-302J-T (AVX)	0603
R <sub>5</sub>	CR10-302J-T (AVX)	0603
V <sub>1</sub>	SMV1265-011 (Skyworks)	SOD-323
V <sub>2</sub>	SMV1265-011 ( Skyworks)	SOD-323

Table 3. Bill of Materials

Figure 8 shows the PCB layout. The board is made of standard FR4 material 60 mils thick.


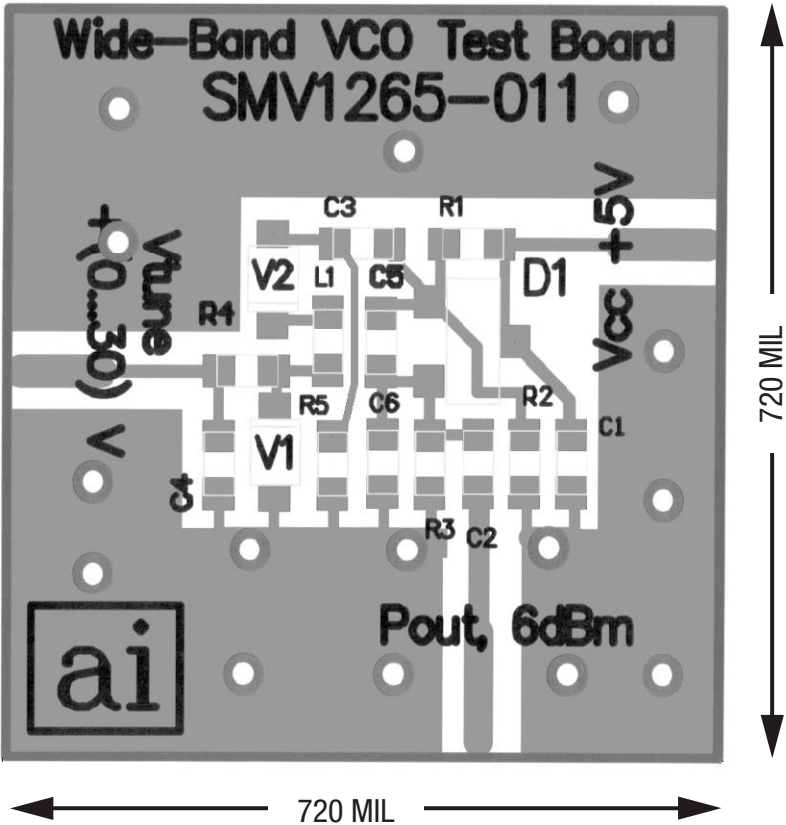


Figure 8. PCB Layout

Figure 9 shows both the measured performance of this circuit and the simulated results, obtained with the above model. The simulated tuning curve (frequency vs. voltage) is in excellent agreement with measured data, proving the effectiveness of the piece-wise approximation technique. The measured power response, shows some differences from its simulation, but is within the same range. A possible reason for the discrepancy could be the effect of higher harmonics. To simulate this would require significantly more complicated modeling of the components, board parasitics, and discontinuities. However, for most engineering purposes, the circuit performance prediction indicated here should be satisfactory.

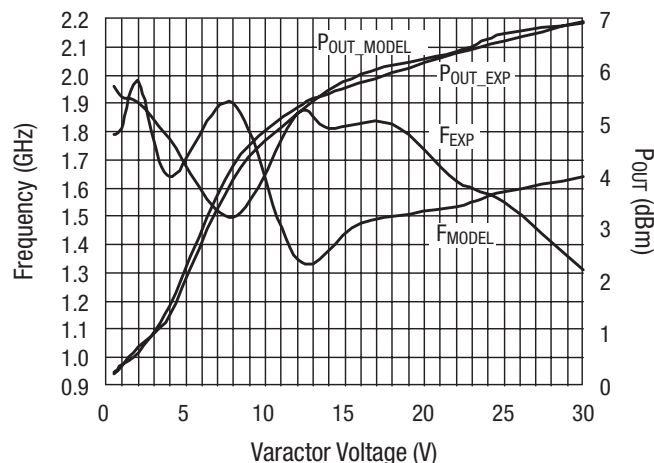

**Figure 9. Measured and Simulated  
Frequency vs. Varactor Voltage**

Table 4 shows tabulated measurement data. In voltage ranges of 1–27 V, the usable frequency coverage was estimated from 0.98–2.15 GHz.

$V_{VAR}$ (V)	Frequency (GHz)	$P_{OUT}$ (dBm)
0.5	0.95	5.7
1	0.974	5.5
2	1.018	5.4
4	1.184	4.7
8	1.68	3.2
12	1.886	5.2
14	1.932	4.9
18	2.008	5
22	2.076	3.9
25	2.12	3.5
30	2.188	2.2

**Table 4. Tabulated Measurement Data**

## List of Available Documents

1. Colpitts Wideband VCO Simulation Project Files for Libra IV.
2. Colpitts Wideband VCO Circuit Schematic and PCB Layout for Protel EDA Client, 1998 version.
3. Colpitts Wideband VCO Gerber Photo-plot Files
4. A Colpitts VCO for Wideband (0.95–2.15 GHz) Set-Top TV Tuner Applications. (Current Document).
5. Detailed measurement and simulation data.

For the availability of the listed materials, please call our applications engineering staff.

© Skyworks Solutions, Inc., 1999. All rights reserved.

Copyright © 2002, 2003, 2004, 2005, Skyworks Solutions, Inc. All Rights Reserved.

Information in this document is provided in connection with Skyworks Solutions, Inc. ("Skyworks") products or services. These materials, including the information contained herein, are provided by Skyworks as a service to its customers and may be used for informational purposes only by the customer. Skyworks assumes no responsibility for errors or omissions in these materials or the information contained herein. Skyworks may change its documentation, products, services, specifications or product descriptions at any time, without notice. Skyworks makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Skyworks assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Skyworks products, information or materials, except as may be provided in Skyworks Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. SKYWORKS DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. SKYWORKS SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Skyworks products are not intended for use in medical, lifesaving or life-sustaining applications, or other equipment in which the failure of the Skyworks products could lead to personal injury, death, physical or environmental damage. Skyworks customers using or selling Skyworks products for use in such applications do so at their own risk and agree to fully indemnify Skyworks for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Skyworks products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Skyworks assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Skyworks products outside of stated published specifications or parameters.

Skyworks, the Skyworks symbol, and "Breakthrough Simplicity" are trademarks or registered trademarks of Skyworks Solutions, Inc., in the United States and other countries. Third-party brands and names are for identification purposes only, and are the property of their respective owners. Additional information, including relevant terms and conditions, posted at [www.skyworksinc.com](http://www.skyworksinc.com), are incorporated by reference.